
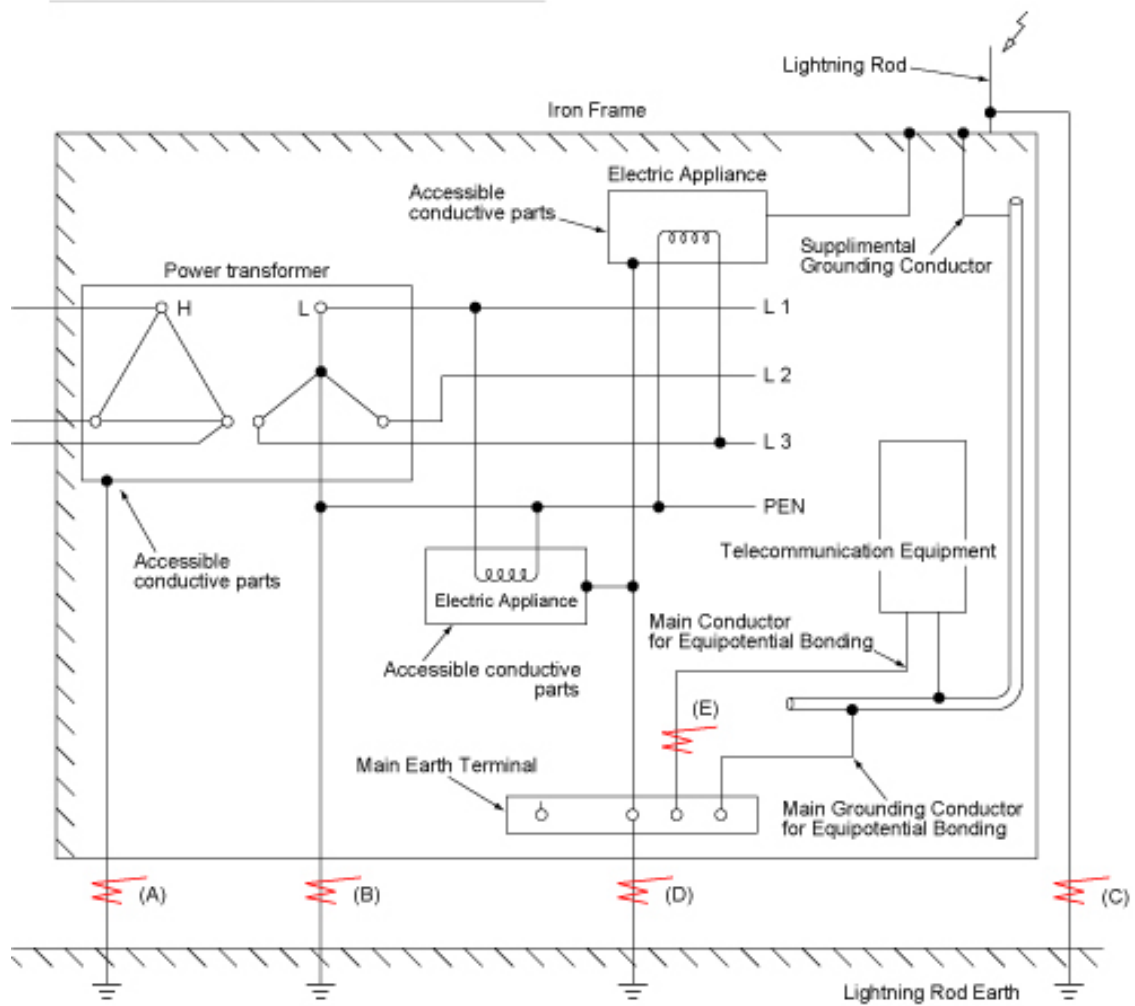



Measuring example of clamp earth tester

 : Clamping point


Measurements of low voltage circuit



Measurements of multi-grounded system

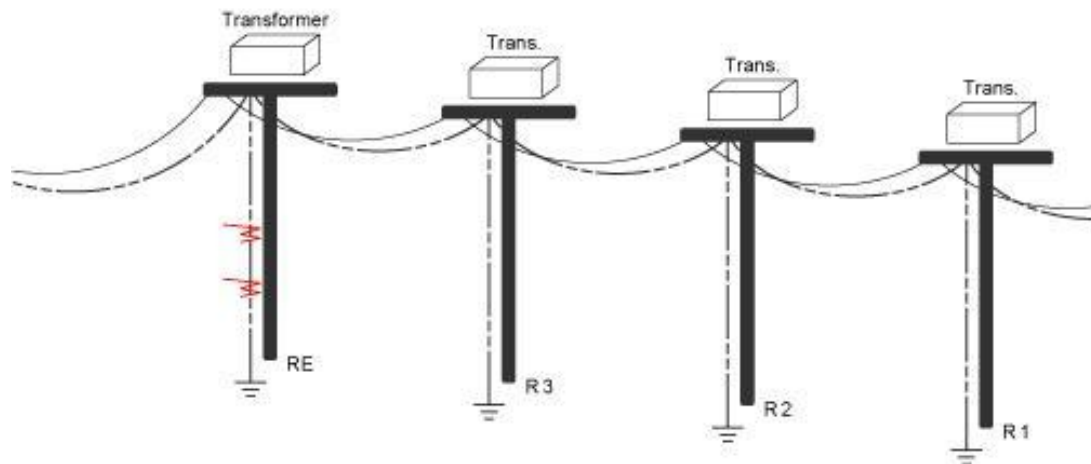

Equivalent circuit

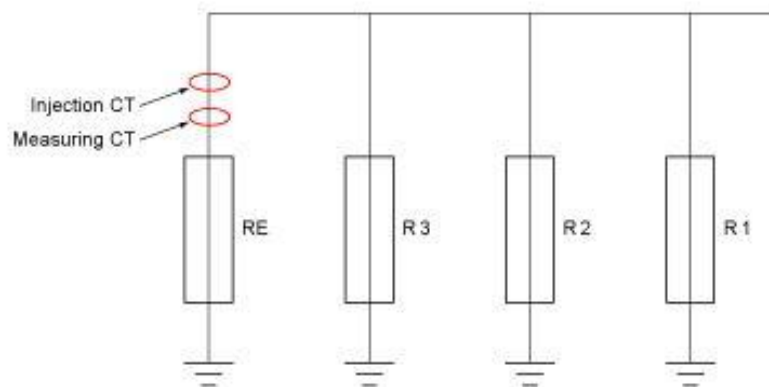

$$\text{Test result} = RE + (R3 // R2 // R1)$$

Resistance of parallel connection $(R3 // R2 // R1) < RE$

$$\text{Test result} \approx RE$$